



Cellular Engine TC35

The extra compact module for voice and data transmission

Application Note: AUDIO Interface

Version: 02.00 Date: 09.05.2001

Technical Support: <u>wm.support@mch.siemens.de</u>

Doc Id: TC35-AN-02-V02.00

Status: Released

Copyright © Siemens AG 2001





Table of contents

| 1 | Introduction | |
|------|--|----|
| | 1.1 References | |
| | 1.2 Terms and Abbreviations | |
| 2 | General | 4 |
| | 2.1 Approval Considerations | 4 |
| 3 | Audio Interface Schematic | 5 |
| | 3.1 Description of the receive path | |
| | 3.2 Description of the transmit path | |
| | 3.2.1 Earpiece stereo jack (X1101) | |
| | 3.2.2 Microphone Signal (X1102) | |
| | 3.3 Handset connector (X1100) | 8 |
| 4 | Power supply for audio interface | 8 |
| 5 | Component lists | g |
| | 5.1 Bill of material (audio interface) | |
| | 5.2 Bill of material (audio power interface) | |
| 6 | Avoiding RF and electromagnetic interferences | 12 |
| • | 6.1 RF Protection | |
| | 6.2 EMC | |
| 7 | Type Approved Handset for TC35 | 12 |
| | | |
| Fig | gures | |
| Figu | ure 1: Audio Interface Schematic on the DSB35 Support Box | 5 |
| Figu | ure 2: Pin assignment - X1101 jack for earpiece signal | 7 |
| | ure 3: Pin assignment – X1102 jack for microphone signal | |
| Figu | ure 4: Analog power supply | 8 |
| Tab | bles | |
| Tabl | ele 1: Pin assignment of the Western jack used for the Handset | 8 |
| | le 2 : Bill of Material (audio Interface) | |

General note

With respect to any damages arising in connection with the described product or this document, Siemens shall be liable according to the General Conditions on which the delivery of the described product and this document are based.

This product is not intended for use in life support appliances, devices or systems where a malfunction of the product can reasonably be expected to result in personal injury. Siemens AG customers using or selling this product for use in such applications do so at their own risk and agree to fully indemnify Siemens for any damages resulting from illegal use or resale.

Applications incorporating the described product must be designed to be in accordance with the technical specifications provided in these guidelines. Failure to comply with any of the required procedures can result in malfunctions or serious discrepancies in results.

Furthermore, all safety instructions regarding the use of mobile technical systems, including GSM products, which also apply to cellular phones must be followed.

Subject to change without notice at any time.





1 Introduction

The purpose of this document is to provide technical recommendations for designing the audio interface intended for a TC35 based cellular application.

Specifications subject to change without notice. This product is an original Siemens product protected by US, European and other patents.

1.1 References

TC35_HW_Interface_description

1.2 Terms and Abbreviations

DSB35 Development Support Box 35
EMC Electro Magnetic Compatibility
EMI Electromagnetic Interference

EPP Ear Peace Positive
EPN Ear Peace Negative
ESD Electrostatic discharge

GSM Global System for Mobile Communication

RF Radio Frequency
MICP Microphone Positive
MICN Microphone Negative
PCB Printed Circuit Board

SIM Subscriber Identifier Module

VANA Voltage Analog VREF Voltage Reference





2 General

The purpose of this document is to provide recommendations for integrating audio accessories into your TC35 application. To give an example, the technical specifications proceed from the certified Siemens reference GSM application that consists of the following components:

- TC35 module
- DSB35 Support box
- Siemens M20 Terminal Handset.

The DSB35 Support Box can be purchased for testing and evaluating GSM applications that incorporate the TC35 module. Click here for more details and ordering information: http://www.siemens.com/wm

2.1 Approval Considerations

For Europe (R&TTE) it is not mandatory to provide an extra approval for the audio equipment that integrates with the TC35 GSM engine. However, should your application be enhanced beyond the certified Siemens reference configuration, it is recommended that you apply for an additional approval.

In other countries, you are required to obtain an extra approval when your audio equipment differs from the audio schematics detailed below.





3 Audio Interface Schematic

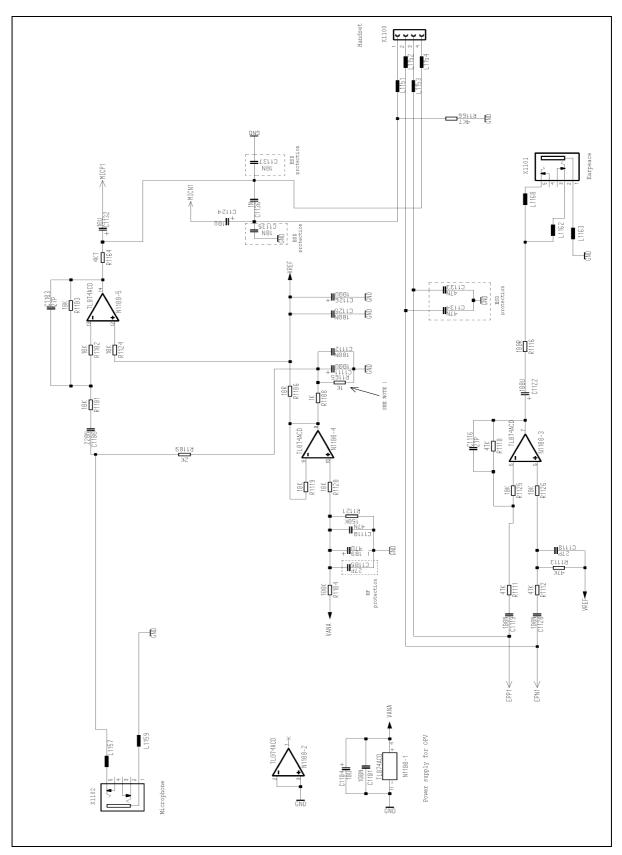


Figure 1: Audio Interface Schematic on the DSB35 Support Box





*) Note (to Figure 1)

The two R1108 (1K) and R1165 (1K) resistors are used as voltage dividers for the microphones. In the schematic both resistors are designed as 1k. This results in 6V for the handset microphone (powered over R1106) and 3V behind R1108 (1K) to supply the external microphone (X1102). By using different resistor values for R1165 you can vary the power supply for your external microphone.

3.1 Description of the receive path

The differential output signal EPP1/EPN1 of the TC35 connects directly to X1100 pin 3 and 2 via the EMI chokes L1153 and L1152.

Two capacitors (C1133 and C1134) protect EPP1/EPN1 against ESD.

In parallel to EPP1/EPN1 the differential amplifier N1100-3 picks up the signal from the TC35 module to the earpiece jack X1101, converting it into an asymmetric output signal to ground. This amplifier with unity gain can drive a stereo headphone plugged into X1101.

The handset itself does not need the amplifier N1100-3.

3.2 Description of the transmit path

The amplifier N1100-5 provides a dc output voltage of 6V for feeding the handset's microphone. This feeding current flows via R1164 (4k7), L1154, X1100 and pin 4 through the microphone. It returns via X1100, pin 1, L1151and R1166 (4k7) to ground.

The differential microphone signal is picked up by the TC35's MICP1 and MICN1 pins through the decoupling capacitors C1132 and C1124.

ESD protection is provided by C1135 to C1137.

An external electret microphone can be connected to jack X1102, which provides a 3V feeding source with a resistance of 2k. This signal is superimposed to the feeding voltage of the handset's microphone by the unity gain amplifier N1100-5.

In applications with the M20T handset and without any external microphone, N1100-5 can be replaced with any 6V dc source.





3.2.1 Earpiece stereo jack (X1101)

The earpiece signal is generated by the audio interface (earpiece signal output, pin 2 and pin 5). The audio interface can be designed as a 3.5 mm stereo connector like the X1101 jack located on the DSB35 Support Box board.

On the DSB35 Support Box board, the X1101 earpiece jack and the X1100 Western jack for the handset are connected in parallel.

The stereo jack connections are shown in Figure 2 below.

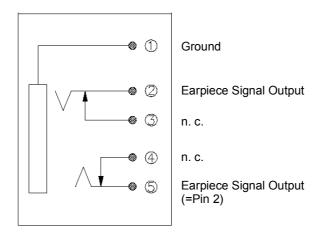


Figure 2: Pin assignment - X1101 jack for earpiece signal

3.2.2 Microphone Signal (X1102)

For the microphone signal, the DSB35 Support Box board uses a 3.5 stereo jack (external mic. input, pin 5). In Figure 1 it is designated X1102.

On the DSB35 Support Box board, the X1102 microphone jack and the X1100 Western jack for the handset are connected in parallel.

The stereo jack connections are shown in Figure 3 below.

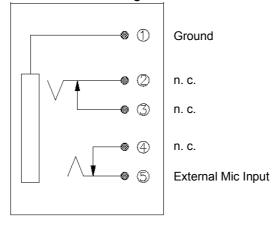


Figure 3: Pin assignment – X1102 jack for microphone signal





3.3 Handset connector (X1100)

To include a handset into your TC35 application, e.g. for audio measurements, you can also follow the specification of the DSB35 Support Box:

The box uses a 4-pin Western jack for this purpose. For the power supply of the microphone there is a voltage of 6V (over 2 x $4.7k\Omega$) available between Pin 4 and pin 1. The pin assignment (pin numbering from left to right) of the Western jack is shown in Table 1 below:

| Signal name | Pin | I/O | Description | |
|-------------|-----|-----|--------------------|--|
| HS_MIC- | 1 | I | Microphone minus | |
| HS_LS- | 2 | 0 | Loudspeaker minus | |
| HS_LS+ | 3 | 0 | Loudspeaker signal | |
| HS_MIC+ | 4 | I | Microphone signal | |

Table 1: Pin assignment of the Western jack used for the Handset

4 Power supply for audio interface

The following schematic illustrates an example of how to design a power supply for the analog power of the audio interface (VANA).

The MAX1683 (Maxim semiconductor) is a voltage doubler. It allows to use the 5V digital power from your host interface to generate the required 10V analog power for the audio part.

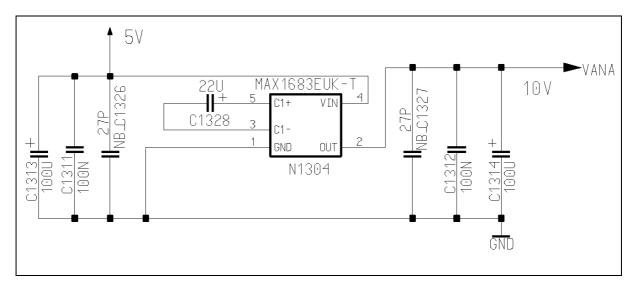


Figure 4: Analog power supply





5 Component lists

5.1 Bill of material (audio interface)

| Pos | Label | Component | -Tol | +Tol | Form | U/P | Others |
|-----|-------|-------------|------|------|----------|-----|---------------|
| 1 | C1100 | 220N | 10% | 10% | 0603 | 10 | |
| 2 | C1101 | 100N | 80% | 20% | 0402 | 16 | |
| 3 | C1103 | 27P | 5% | 5% | 0402 | 25 | |
| 4 | C1104 | 10U | 20% | 20% | Tantal A | 10 | |
| 5 | C1105 | 27P | 2% | 2% | 0402 | 25 | RF protection |
| 7 | C1109 | 47U | 20% | 20% | Tantal D | 16 | |
| 8 | C1110 | 47N | 10% | 10% | 0805 | 25 | |
| 9 | C1111 | 100U | 20% | 20% | Tantal D | 16 | |
| 10 | C1112 | 100N | 80% | 20% | 0402 | 16 | |
| 11 | C1116 | 27P | 5% | 5% | 0402 | 25 | |
| 12 | C1118 | 27P | 5% | 5% | 0402 | 25 | |
| 13 | C1119 | 100N | 80% | 20% | 0402 | 16 | |
| 14 | C1120 | 100N | 80% | 20% | 0402 | 16 | |
| 15 | C1122 | 100U | 20% | 20% | Elko E | 25 | |
| 16 | C1124 | 10U | 20% | 20% | Tantal A | 10 | |
| 17 | C1125 | 100N | 20% | 20% | 0402 | 16 | |
| 18 | C1126 | 100U | 20% | 20% | Tantal E | 16 | |
| 21 | C1132 | 10U | 20% | 20% | Tantal A | 10 | |
| 22 | C1133 | 47N | 10% | 10% | 0805 | 25 | |
| 23 | C1134 | 47N | 10% | 10% | 0805 | 25 | |
| 24 | C1135 | 10N | 10% | 10% | 0603 | 50 | |
| 25 | C1136 | 1N | 5% | 5% | 0603 | 25 | |
| 26 | C1137 | 10N | 10% | 10% | 0603 | 50 | |
| 27 | L1151 | 600R/100MHZ | 0% | 0% | 0805 | | Murata |
| 28 | L1152 | 600R/100MHZ | 0% | 0% | 0805 | | Murata |
| 29 | L1153 | 600R/100MHZ | 0% | 0% | 0805 | | Murata |
| 30 | L1154 | 600R/100MHZ | 0% | 0% | 0805 | | Murata |
| 31 | L1157 | 600R/100MHZ | 0% | 0% | 0805 | | Murata |
| 32 | L1159 | 600R/100MHZ | 0% | 0% | 0805 | | Murata |
| 33 | L1160 | 600R/100MHZ | 0% | 0% | 0805 | | Murata |
| 34 | L1162 | 600R/100MHZ | 0% | 0% | 0805 | | Murata |





| Pos | Label | Component | -Tol | +Tol | Form | U/P | Others |
|-----------|---------|-------------|------|------|---------------------|-----|-----------------------|
| 35 | L1163 | 600R/100MHZ | 0% | 0% | 0805 | | Murata |
| 36 | N1100-1 | TL074ACD | - | - | SO14 | | Texas Instrument |
| 37 | N1100-2 | TL074ACD | - | - | SO14 | | Texas Instrument |
| 38 | N1100-3 | TL074ACD | - | - | SO14 | | Texas Instrument |
| 39 | N1100-4 | TL074ACD | - | - | SO14 | | Texas Instrument |
| 40 | N1100-5 | TL074ACD | - | - | SO14 | | Texas Instrument |
| 41 | R1101 | 10K | 1% | 1% | 0402 | | |
| 42 | R1102 | 10K | 5% | 5% | 0402 | | |
| 43 | R1103 | 10K | 5% | 5% | 0402 | | |
| 44 | R1104 | 100K | 1% | 1% | 0402 | | |
| 45 | R1106 | 10R | 2% | 2% | 0805 | | |
| 47 | R1108 | 1K | 5% | 5% | 0402 | | |
| 48 | R1109 | 2K | 2% | 2% | 0603 | | |
| 49 | R1110 | 47K | 5% | 5% | 0402 | | |
| 50 | R1111 | 47K | 5% | 5% | 0402 | | |
| 51 | R1112 | 47K | 5% | 5% | 0402 | | |
| 52 | R1113 | 47K | 5% | 5% | 0402 | | |
| 54 | R1116 | 100R | 2% | 2% | 0805 | | |
| 57 | R1119 | 10K | 5% | 5% | 0402 | | |
| 58 | R1120 | 10K | 5% | 5% | 0402 | | |
| 59 | R1121 | 150K | 1% | 1% | 0402 | | |
| 60 | R1123 | 10K | 5% | 5% | 0402 | | |
| 61 | R1124 | 10K | 5% | 5% | 0402 | | |
| 62 | R1125 | 10K | 5% | 5% | 0402 | | |
| 63 | R1126 | 10K | 5% | 5% | 0402 | | |
| 64 | R1164 | 4K7 | 1% | 1% | 0603 | | |
| 65 | R1165 | 1K | 1% | 1% | 0402 | | See note in Chapter 3 |
| 66 | R1166 | 4K7 | 5% | 5% | 0402 | | |
| 67 | X1100 | 4-POL | - | - | 4P4C Western | | |
| 68 | X1101 | 5-POL | - | - | 5pol stereo jack | | |
| 69 | X1102 | 5-POL | - | - | 5pol stereo jack | | |

Table 2 : Bill of Material (audio Interface)





5.2 Bill of material (audio power interface)

| Pos | Label | Component | -Tol | +Tol | Form | U/P | Others |
|-----|-------|-------------------|------|------|----------|-----|---------------|
| 1 | N1304 | MAX1683- EUK-T | - | - | SOT23-5 | | Maxim |
| 2 | C1311 | 100N | 80% | 20% | 0805 | 25 | |
| 3 | C1312 | 100N | 80% | 20% | 0805 | 25 | |
| 4 | C1313 | 100U | 80% | 20% | Tantal E | 16 | |
| 5 | C1314 | 100U | 20% | 20% | Tantal E | 16 | |
| 6 | C1326 | 27P | 2% | 2% | 0402 | 25 | RF protection |
| 7 | C1327 | 27P | 2% | 2% | 0402 | 25 | RF protection |
| 8 | C1328 | 22U | 20% | 20% | Tantal D | 25 | |





6 Avoiding RF and electromagnetic interferences

6.1 RF Protection

In order to prevent your TC35 application from causing RF interference across the audio path, you may be required to add capacitors on the PCB.

For the layout of your application it is essential, that these capacitors are located close to the pins to be protected.

Example

Capacitors placed on the board of the DSB35 Support Box:

- Audio Schematics C1105
- Audio Power Schematics C1326, C1327

6.2 EMC

To ensure that your TC35 application meets EMC requirements, it is recommended to add inductors for protecting external connectors.

For the layout of your application it is essential, that these inductors are located close to the connectors they are required for.

The inductors can be replaced with zero Ohm resistors.

Example

Inductors placed on the board of the DSB35 Support Box:

L1151,L1152, L1153, L1154, L1157, L1159, L1159, L1160, L1162, L1163

7 Type Approved Handset for TC35

The M20 Terminal handset is used as the reference handset in conjunction with the DSB35 Support Box and the TC35 module and, therefore, forms part of the certified Siemens reference configuration for TC35.

This passive handset requires a power supply for the microphone as shown in Figure 1. An adapter amplifier (Figure 1) and the power supply (Figure 4) required for the handset are available on the DSB35 Support Box.

Other handset types you may want to integrate into your TC35 application are not covered by the approval issued for the Siemens reference configuration. You may therefore be required to achieve an extra approval for specific handsets or audio equipment (see also Chapter 2).

Odering information

M20 Terminal Handset (Siemens product no. S30880-S8001-A300-1)